

Seat No.	
-------------	--

B.Sc. (Part - III) (Semester - V) (CBCS)**Examination, January-2023****PHYSICS (Paper-XII)****DSE-E4 : Digital and Analog Circuits and Instrumentation****Subject Code: 79680****Day and Date : Friday, 06 - 01 - 2023****Total Marks : 40****Time : 2.30 p.m. to 4.30 p.m.**

- Instructions :**
- 1) All questions are compulsory.
 - 2) Figures to the right indicate full marks.
 - 3) Neat diagrams must be drawn whenever necessary.
 - 4) Use of calculators/logarithmic tables are allowed.

Q1) Select correct alternative.**[8]**

- a) _____ is a logic circuit that adds two binary digit at a time.
- i) full addder
 - ii) half addder
 - iii) flip flop
 - iv) gates
- b) For_____gate output is high when all its inputs are low.
- i) NOR
 - ii) NAND
 - iii) XOR
 - iv) AND
- c) In digital circuit_____represents a binary low level.
- i) binary one
 - ii) binary zero
 - iii) binary two
 - iv) binary infinite
- d) The current amplification factor in a common emitter configuration is the ratio of_____
- i) $\Delta I_E / \Delta I_B$
 - ii) $\Delta I_B / \Delta I_E$
 - iii) $\Delta I_C / \Delta I_B$
 - iv) $\Delta I_C / \Delta I_E$
- e) Astable multivibrator has_____stable states.
- i) two
 - ii) three
 - iii) one
 - iv) zero

P.T.O.

- f) In CE transistor amplifier circuit input is applied to _____ terminal of the transistor.
- | | |
|----------------|-------------------|
| i) base | ii) emitter |
| iii) collector | iv) none of these |
- g) The arrangement of electrodes which produce a focused beam of electrons is called _____.
- | | |
|--------------------|-------------------|
| i) electron tube | ii) electron gun |
| iii) electric tube | iv) soldering gun |
- h) The CRO is used to measure _____
- | | |
|------------|------------------|
| i) voltage | ii) frequency |
| iii) phase | iv) all of above |

Q2) Attempt any Two of the following. [16]

- Explain NAND, NOR, Ex-OR and EX-NOR gate with its logic diagram.
- Draw the neat block diagram of CRO and explain the function of each block.
- Draw circuit diagram of astable multivibrator and explain its working. Find the frequency and duty cycle of this multivibrator.

Q3) Write short notes on any four of the following. [16]

- Explain NAND as a universal gate.
- Write a note on half adder.
- Write a note on crystal oscillator.
- Write a note on Lissajous figures with examples.
- State Characteristics of an ideal op-amp.
- Gives advantages and disadvantages of CE amplifier.

